
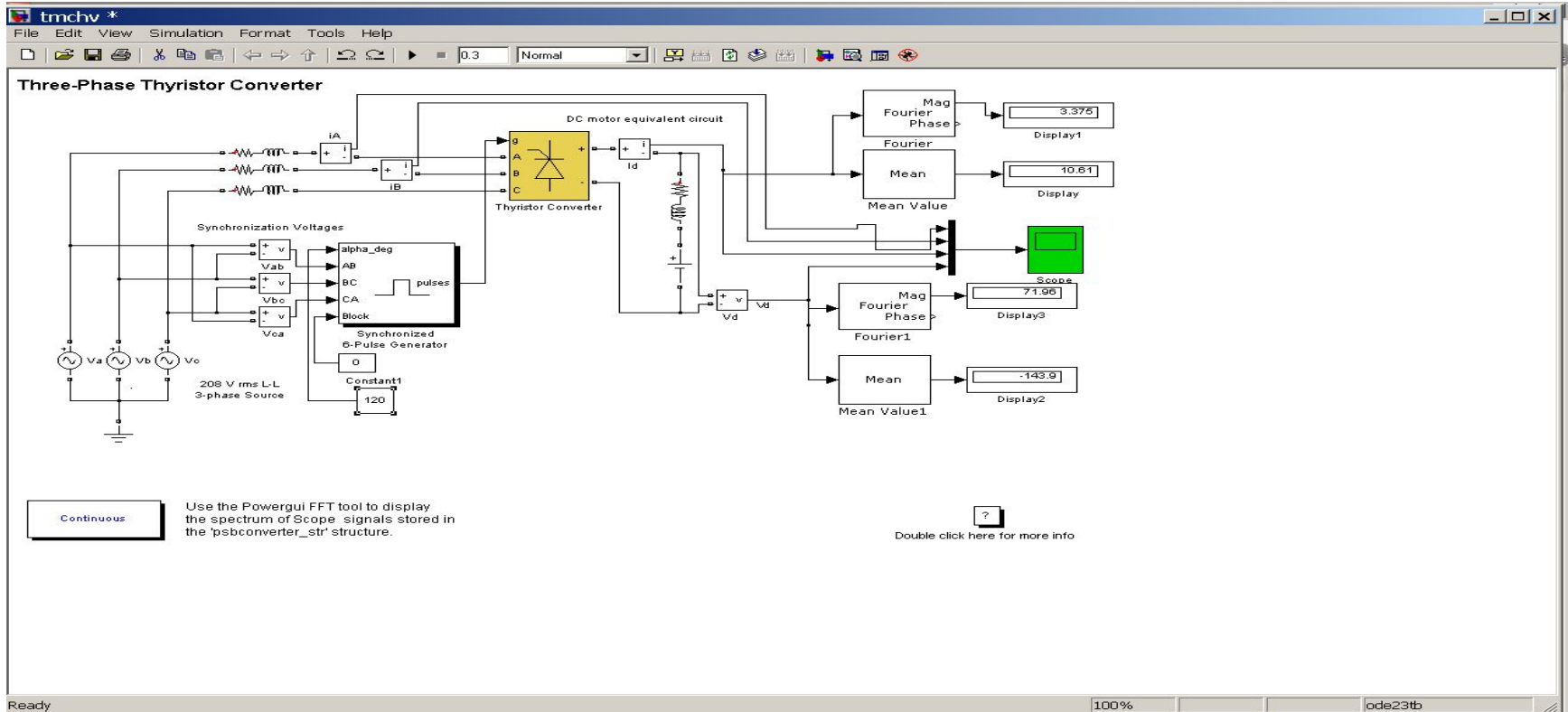



-250

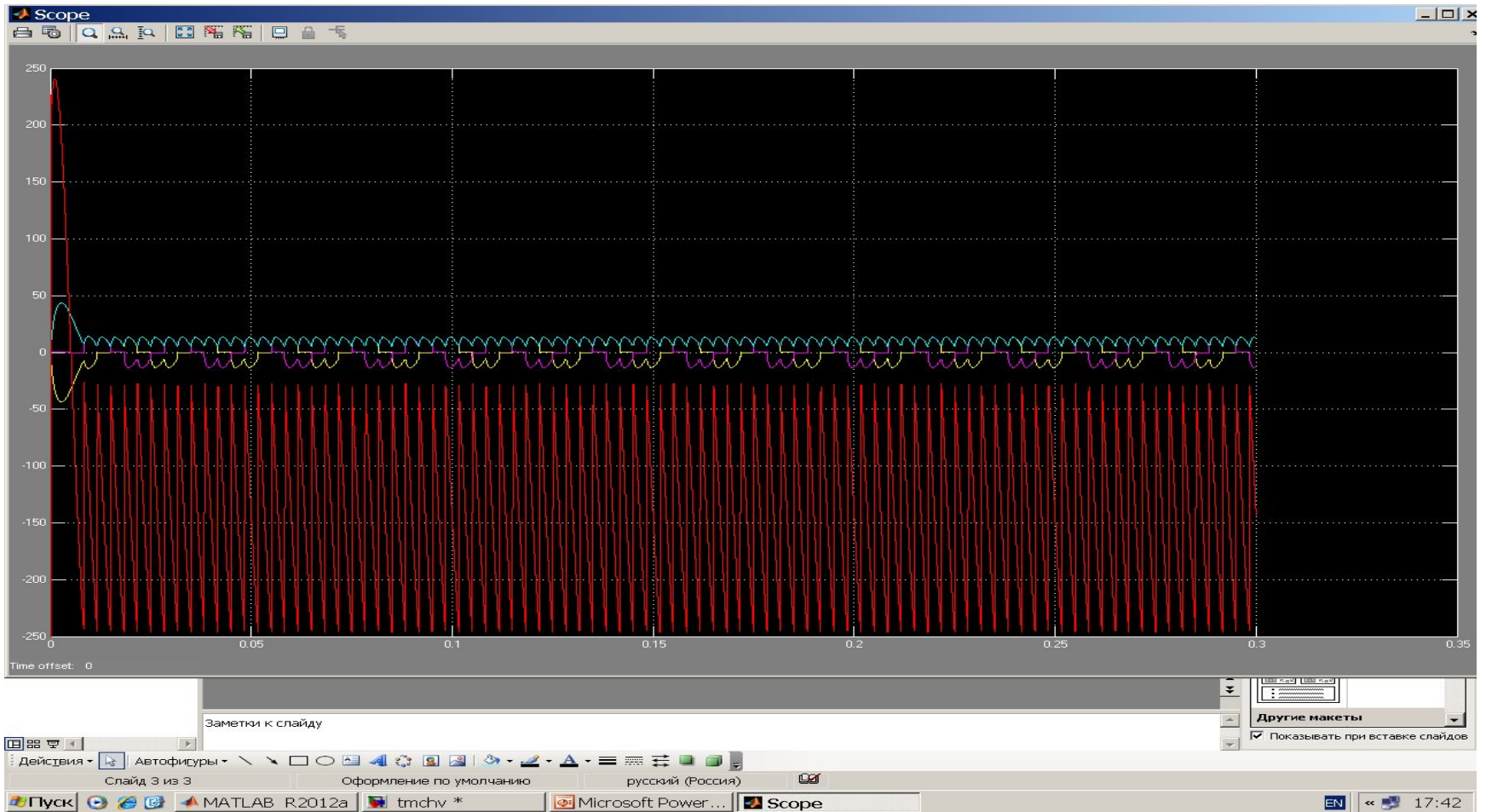


-250/1




-250/2

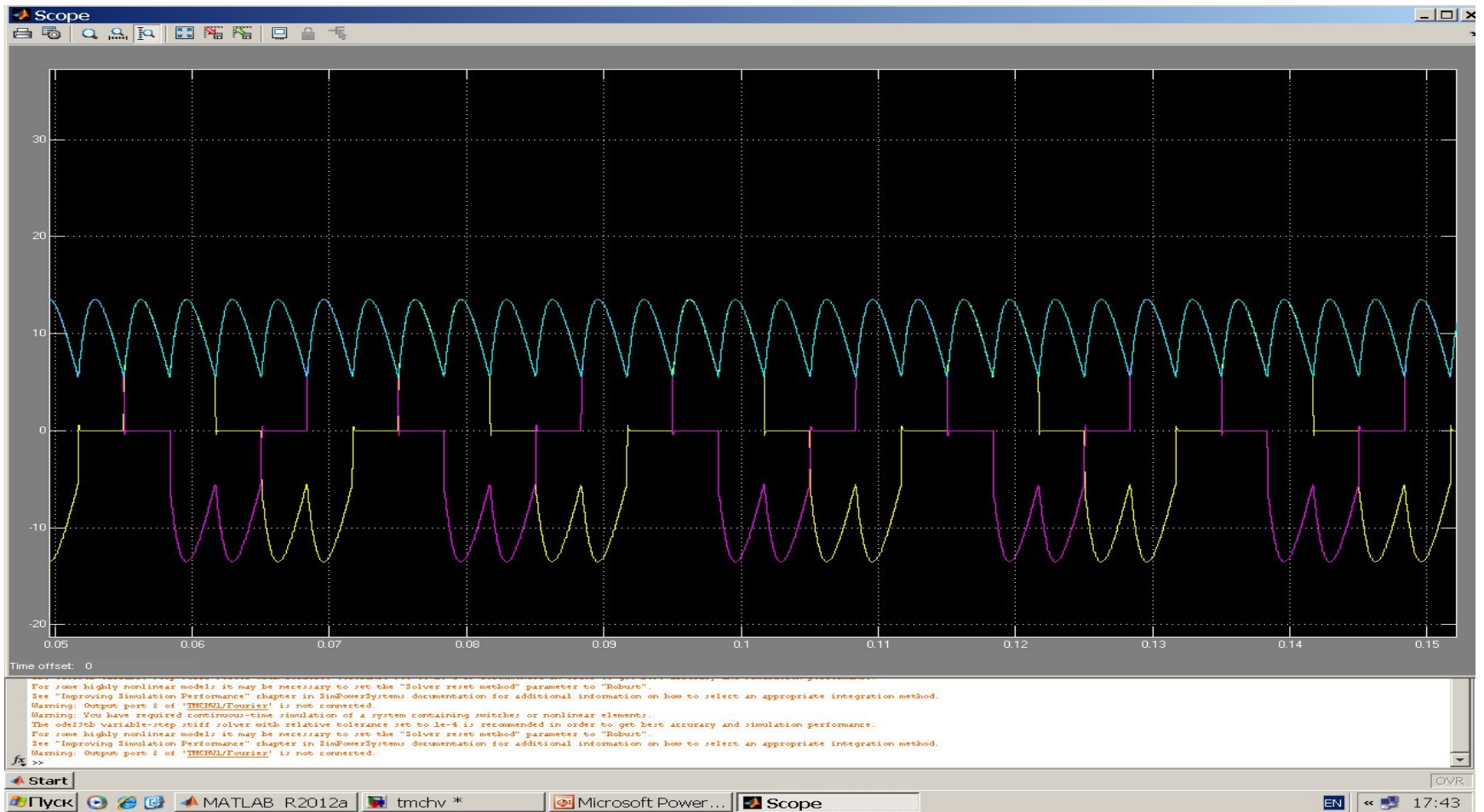


-250/3

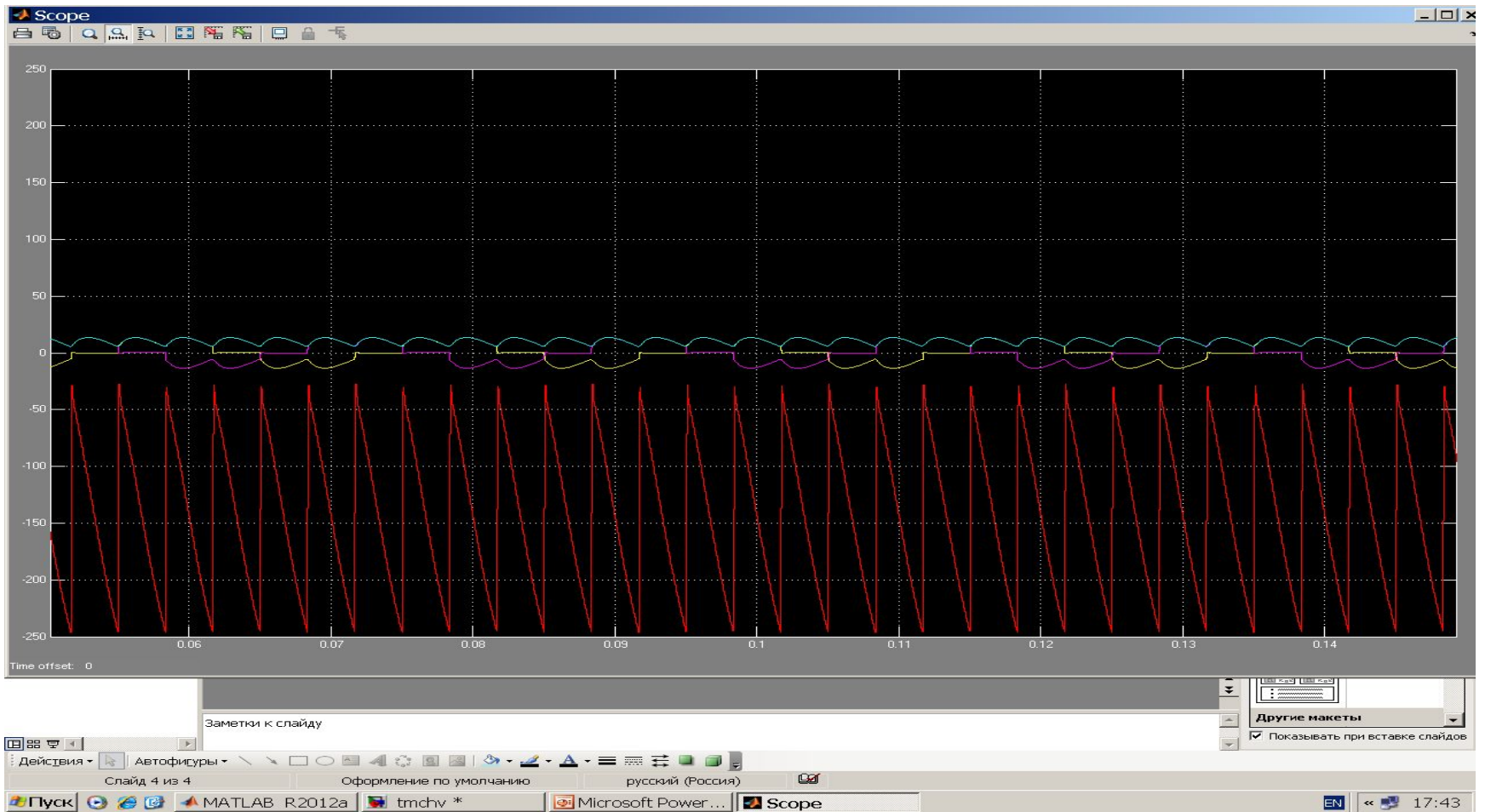


-200

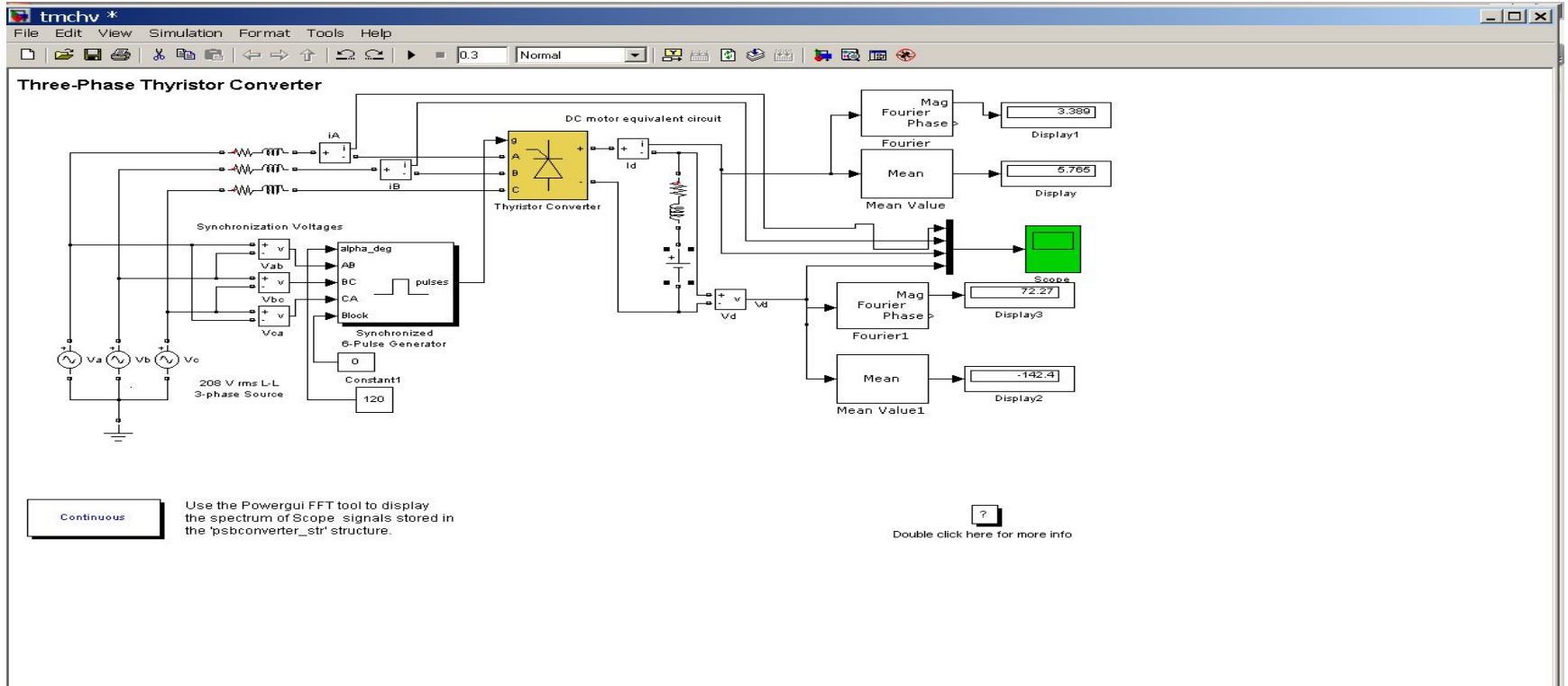


-200/1

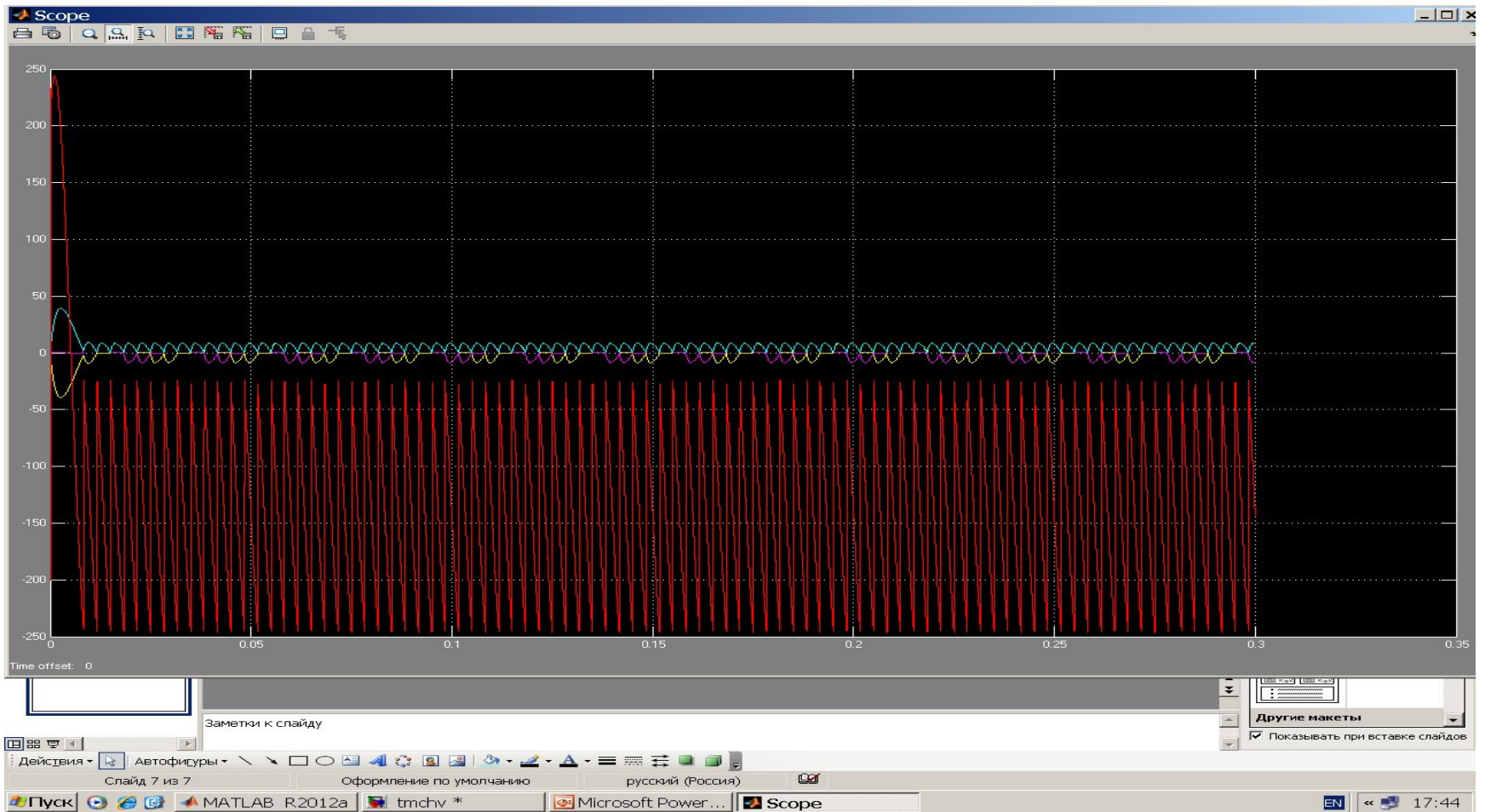

-200/2

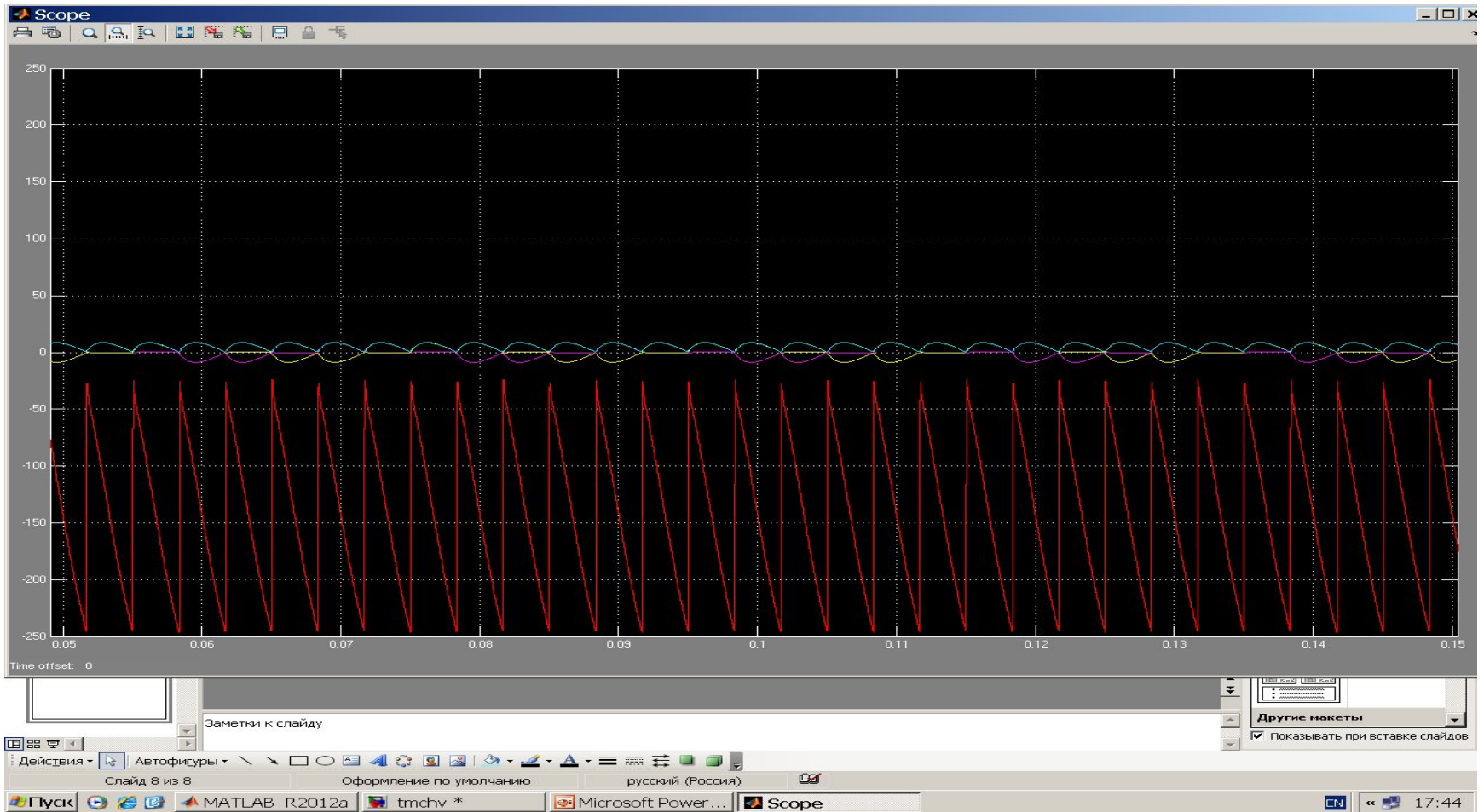

-200/3

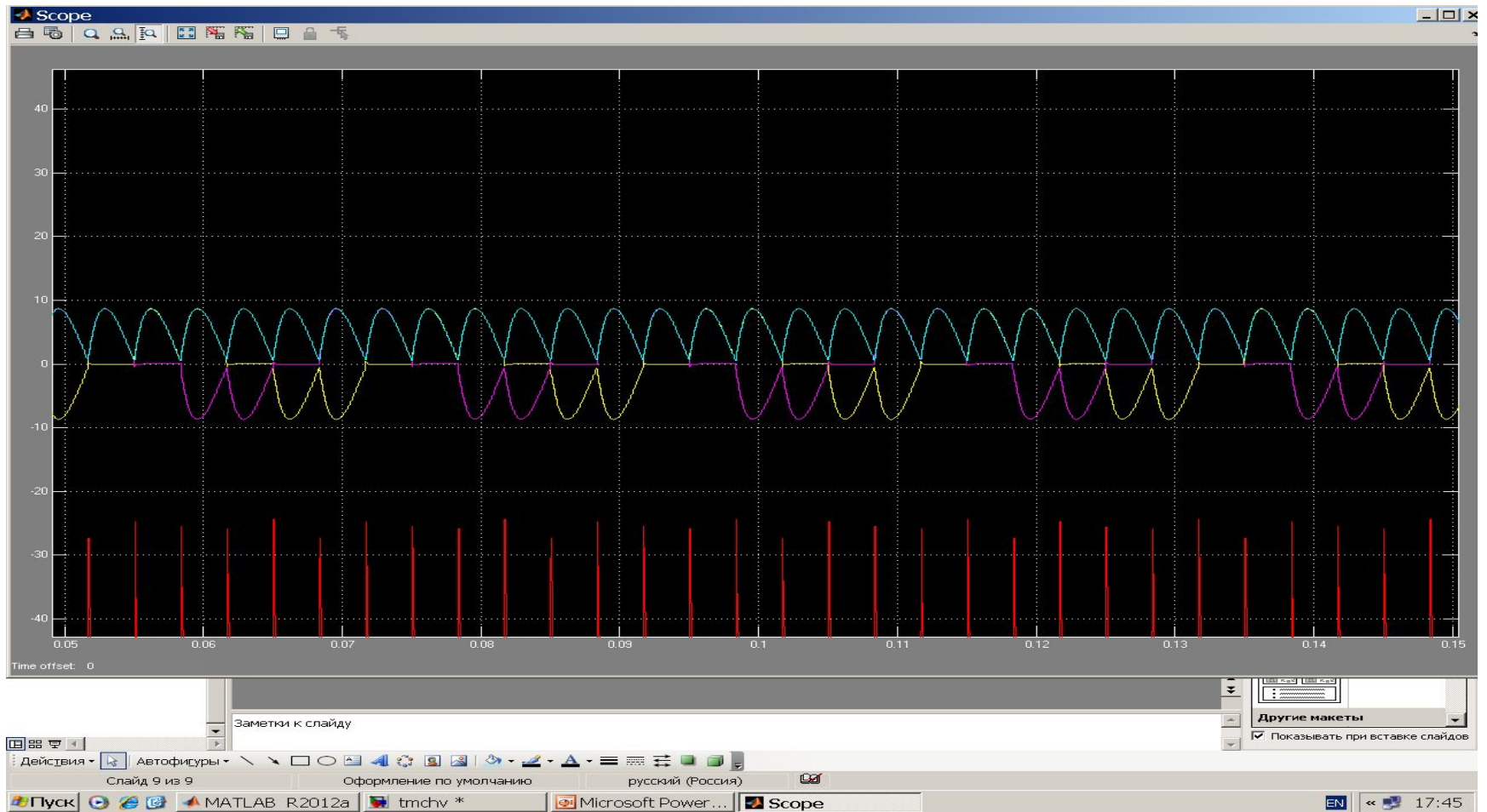

-150

Three-Phase Thyristor Converter

208 V rms L-L 3-phase Source

Synchronization Voltages

alpha_deg

AB

BC

CA

Vca

Block

Synchronized 6-Pulse Generator

Constant1

120

DC motor equivalent circuit

Thyristor Converter

iA

iB

iF

vD

Mag Fourier Phase

Fourier

Mean Value

Mean Value

Scope

Mag Fourier Phase

Fourier1

Mean Value1

Mean Value1

Display1

Display

Display3

Display2

Continuous

Use the Powergui FFT tool to display the spectrum of Scope signals stored in the 'psbconverter_str' structure.

Double click here for more info

Ready 100% ode23tb

Заметки к слайду

Другие макеты

Показывать при вставке слайдов


Слайд 10 из 10

Оформление по умолчанию


русский (Россия)

Пуск MATLAB R2012a tmchv * Microsoft Power... Scope 17:46


-150/1

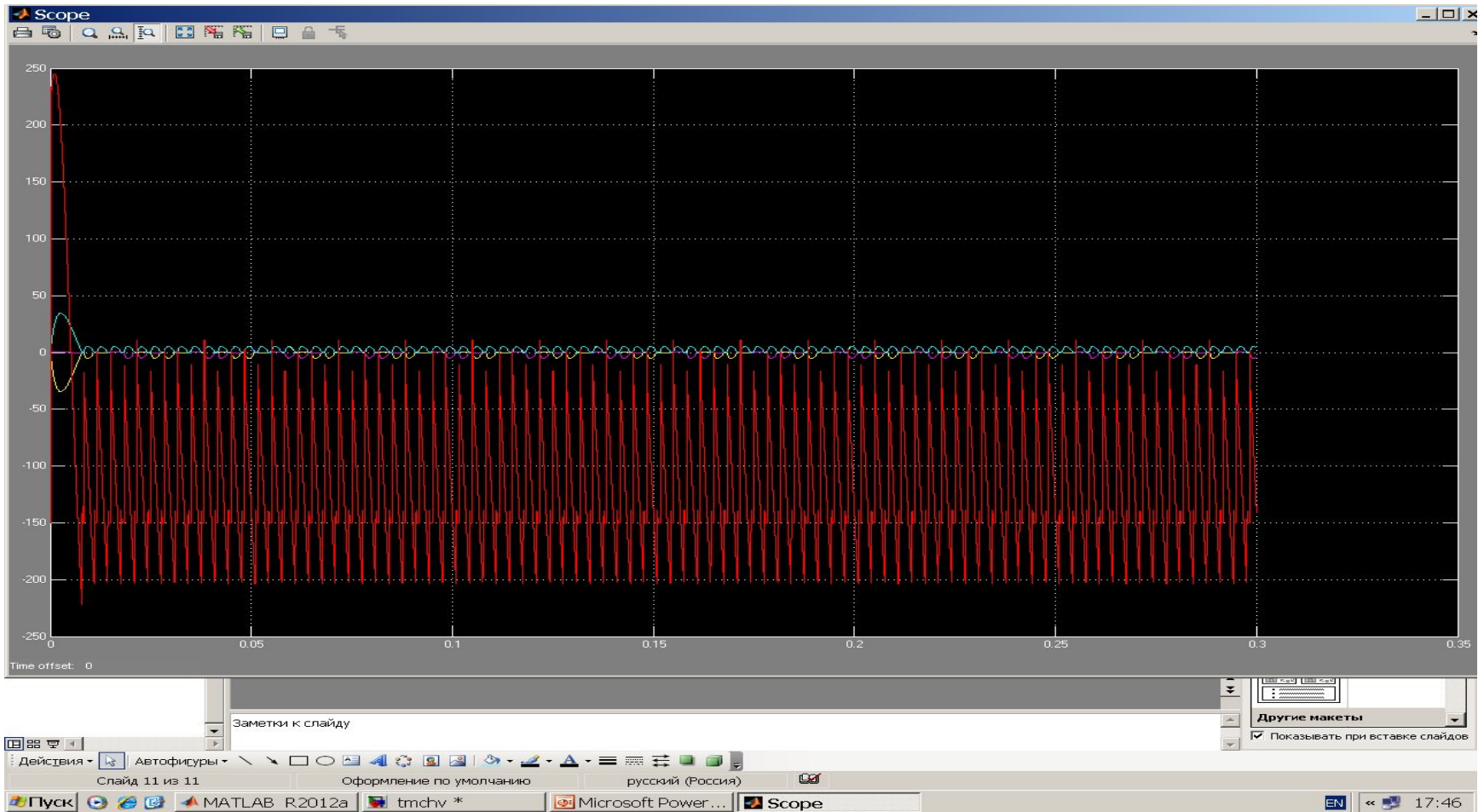

-150/2

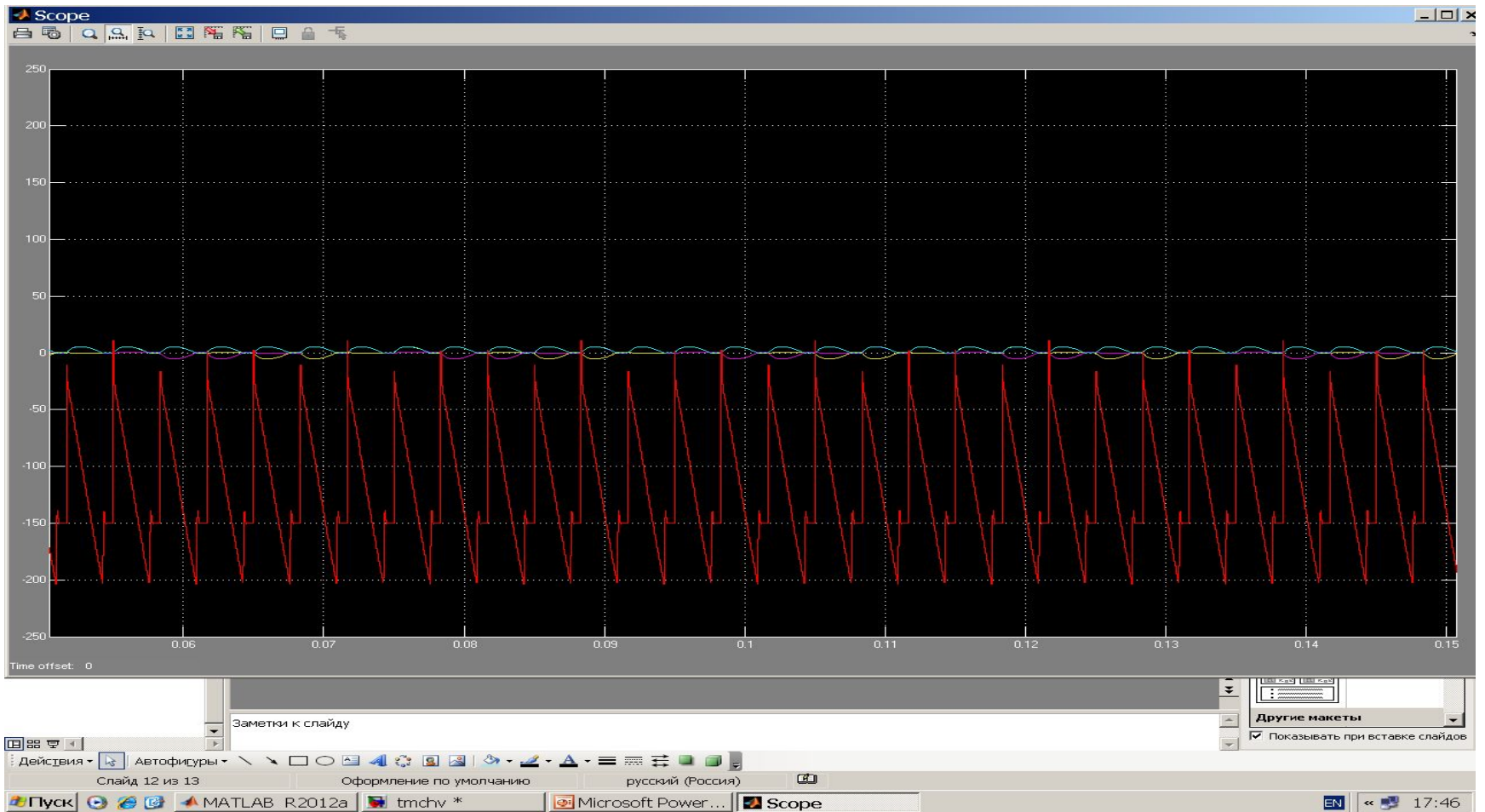

-150/3

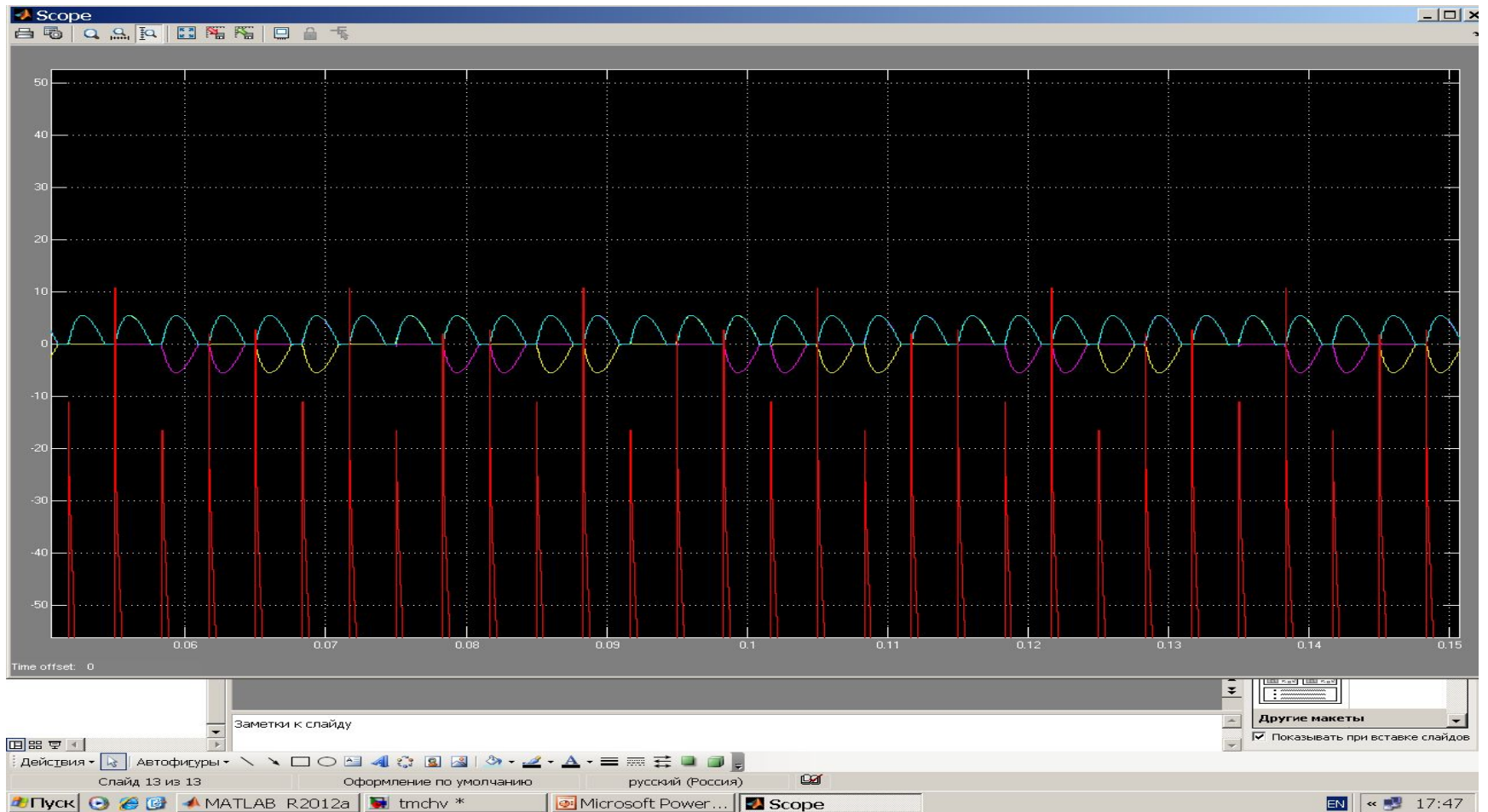

-50

Three-Phase Thyristor Converter

208 V rms L-L 3-phase Source

Synchronization Voltages

alpha_deg

AB

BC

CA

Block

Synchronized 6-Pulse Generator

Constant1

120

Thyristor Converter

DC motor equivalent circuit

Mag Fourier Phase

Fourier

Mean Value

Mean

Scope

Mag Fourier Phase

Fourier1

Mean Value1

Mean

Display1

Display

Display3

Display2

Continuous

Use the Powergui FFT tool to display the spectrum of Scope signals stored in the 'psbconverter_str' structure.

Double click here for more info

Ready

100%

ode23tb

Заметки к слайду

Другие макеты

Показывать при вставке слайдов

Слайд 14 из 16

Оформление по умолчанию

русский (Россия)

Пуск

MATLAB R2012a

tmchv *


Microsoft Power...

Scope


EN

17:47

-50/1

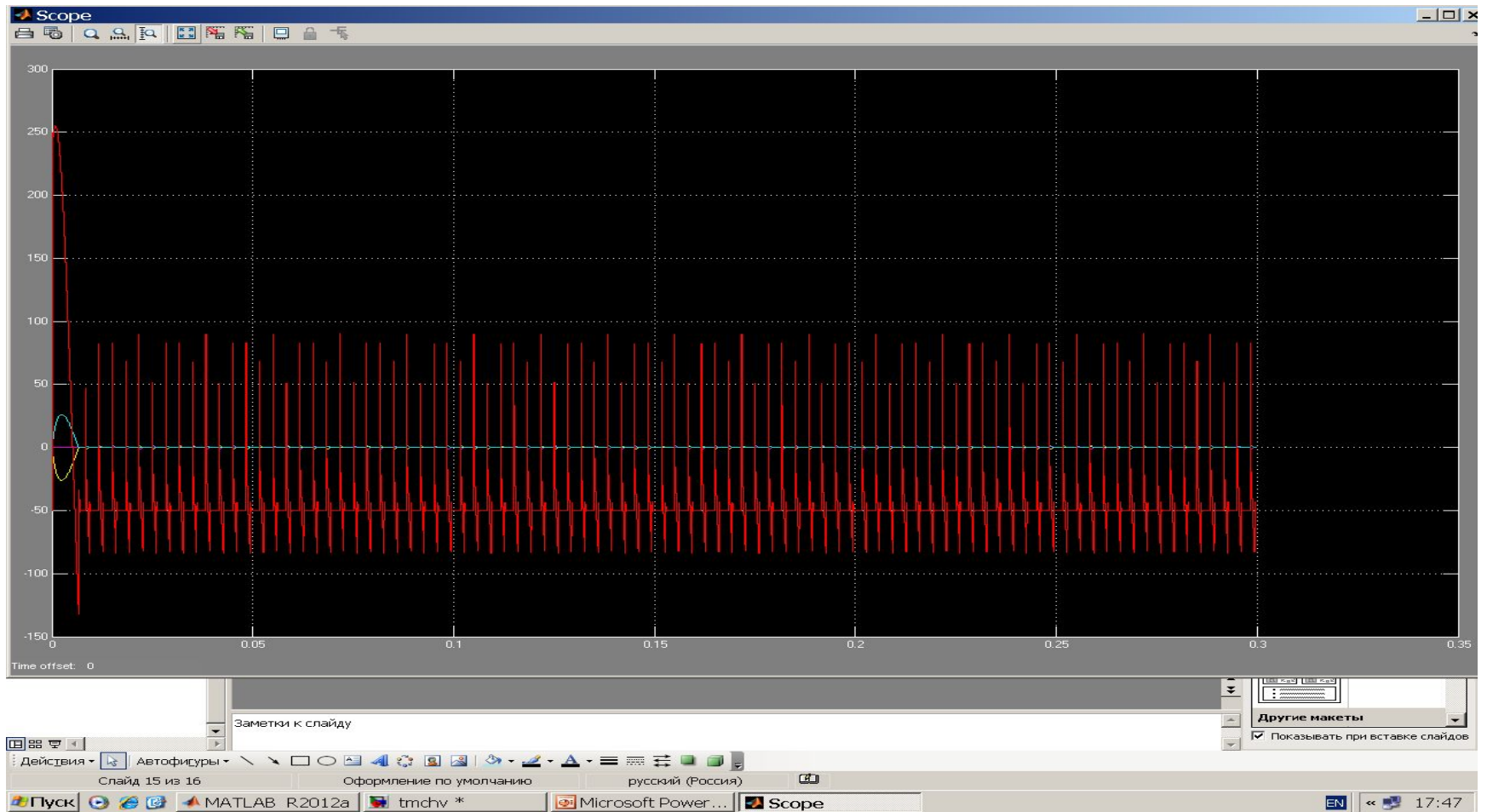

-50/3

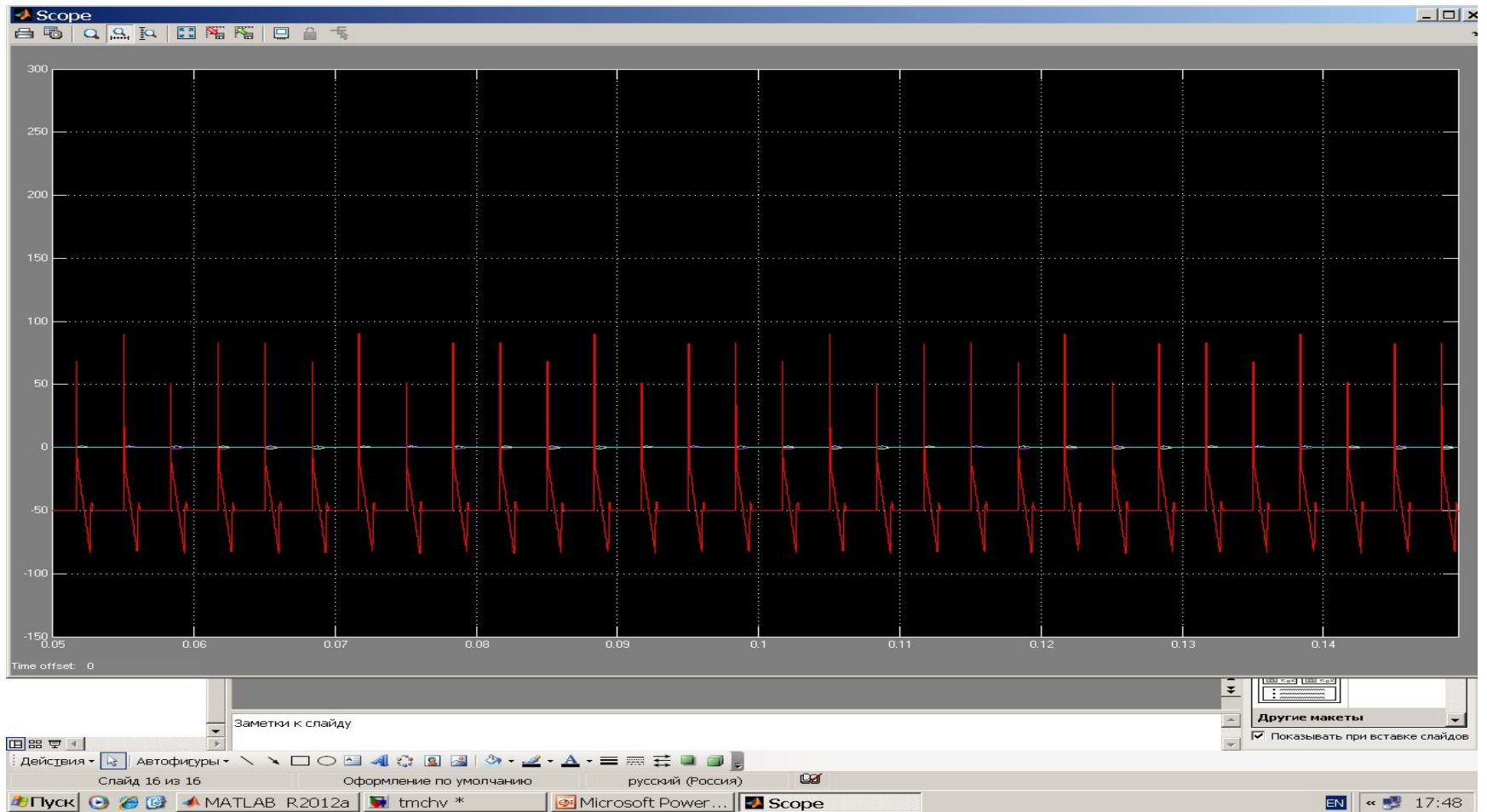

-50/2

