

Другие логические элементы

Определения


- Триггер
- Регистр
- Сумматор
- АЦП (ADC)
- ЦАП (DAC)

Триггер – Flip-Flop

- Триггер- ждущий мультивибратор
- Много есть типов
- Основные – три типа : Flip-Flops
SR, RS , D или JK

SR Flip-Flop- ТРИГГЕР

 The SR flip-flop has two output terminals Q and \overline{Q} . The diagram shows the SR flip-flop using NAND gates.



SR FLIP-FLOP

So basically the flip-flop can exist in two stable states:

$$Q = 1 \ (\overline{Q} = 0) \ \text{or} \ Q = 0 \ (\overline{Q} = 1).$$

SR Flip-Flop- ТРИГГЕР

When $S = 1$ $R = 0$ $Q = 1$ $\bar{Q} = 0$ the flip flop is SET

When $S = 0$ $R = 1$ $Q = 0$ $\bar{Q} = 1$ the flip flop is RESET

When $S = 0$ $R = 0$ then no change occurs Q and \bar{Q} will be what they were before.

When $S = 1$ and $R = 1$ then $Q = 1$ and \bar{Q} equals 1. The circuit is stable while $S = R = 1$, but if they are changed simultaneously from 1 to 0 then due to different switching times of the gates we cannot predict whether Q or \bar{Q} will be 1.

The output state is said to be indeterminate so $S = R = 1$ should not be allowed to occur. The truth table is shown below.

Таблица FLIP-FLOP SR

S	R	Q	\overline{Q}
1	0	1	0
0	1	0	1
0	0	Depends on state before inputs applied	
1	1	Indeterminate	



So basically the flip-flop can exist in two stable states:

$$Q = 1 (\overline{Q} = 0) \text{ or } Q = 0 (\overline{Q} = 1).$$

So basically the flip-flop can exist in two stable states:

$$Q = 1 (\overline{Q} = 0) \text{ or } Q = 0 (\overline{Q} = 1).$$

Clocks

  

DRAWING SYMBOL

CLOCKED SR FLIP FLOP



Clocks

INPUTS		DURING CLOCK PULSE		OUTPUTS BEFORE CLOCK PULSE		OUTPUTS AFTER CLOCK PULSE		COMMENTS
S	R	A	B	Q	\bar{Q}	Q	\bar{Q}	
0	0	1	1	1	0	1	0	NO CHANGE IN OUTPUTS
0	0	1	1	1	0	1	0	
1	0	0	1	1	0	1	0	FLIP-FLOP SETS WITH $\bar{Q} = 0$
1	0	0	1	0	1	1	0	
0	1	1	0	1	0	0	1	FLIP-FLOP RESETS WITH $\bar{Q} = 1$
0	1	1	0	0	1	0	1	
1	1	0	0	1	0	1	1	THIS INPUT IS NOT ALLOWED
1	1	0	0	0	1	1	1	

TRUTH TABLE CLOCKED SR FLIP-FLOP

CLOCKED D- TYPE FLIP-FLOP


This is a modified SR flip-flop.

  


DRAWING SYMBOL

CLOCKED D TYPE FLIP-FLOP

JK FLIP - FLOP

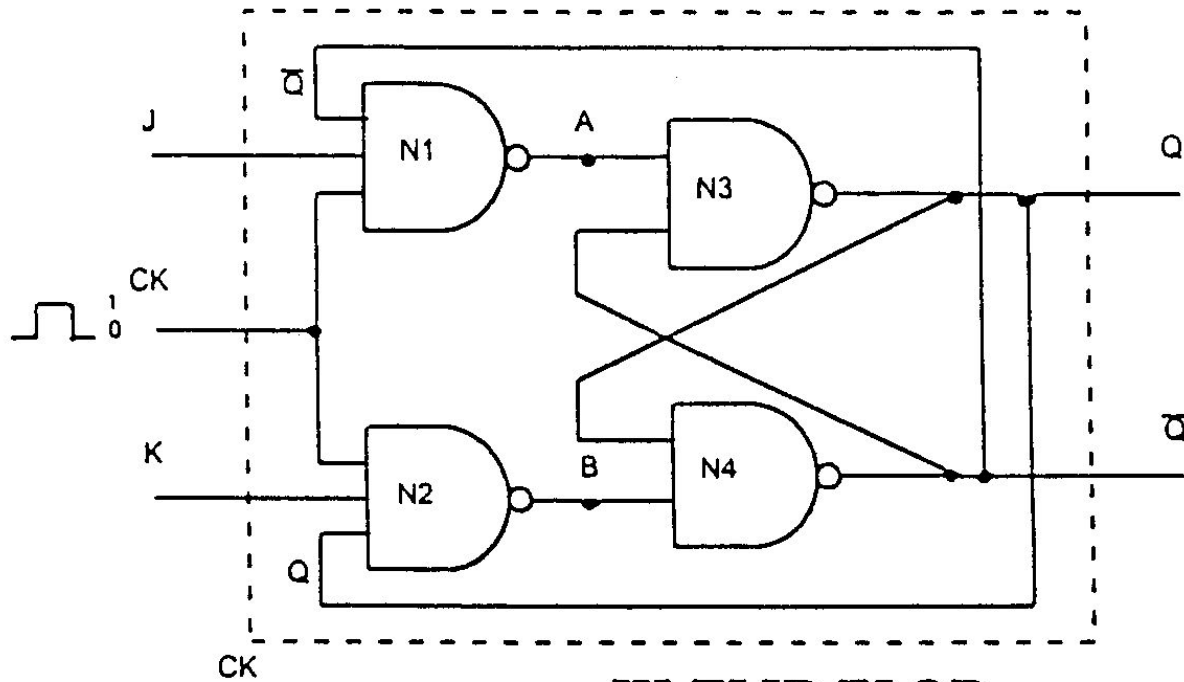


JK FLIP-FLOP

 



DRAWING SYMBOL

Эти триггеры используются в счётчиках и регистрах сдвига

Counters – Счётчики

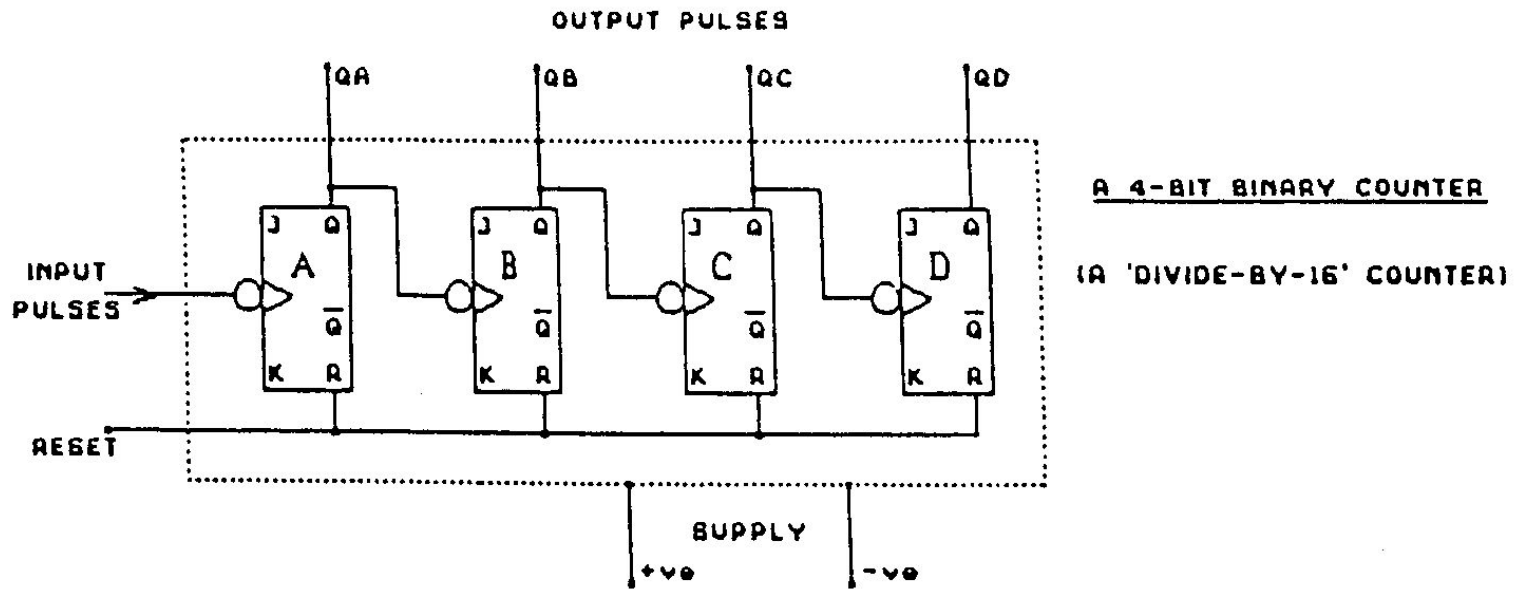

  
После 1-го импульса : $Q_A=1$; $Q_B=0$; $Q_C=0$; $Q_D=0$; 0001 десят. 1
После 2-го импульса : $Q_A=0$; $Q_B=1$; $Q_C=0$; $Q_D=0$; 0010 десят. 2
Когда счётчик достигнет 1111 десятичн. 15 - сброс регистров



FOUR BIT BINARY COUNTER

BACK
TO
START

РЕГИСТР СДВИГА

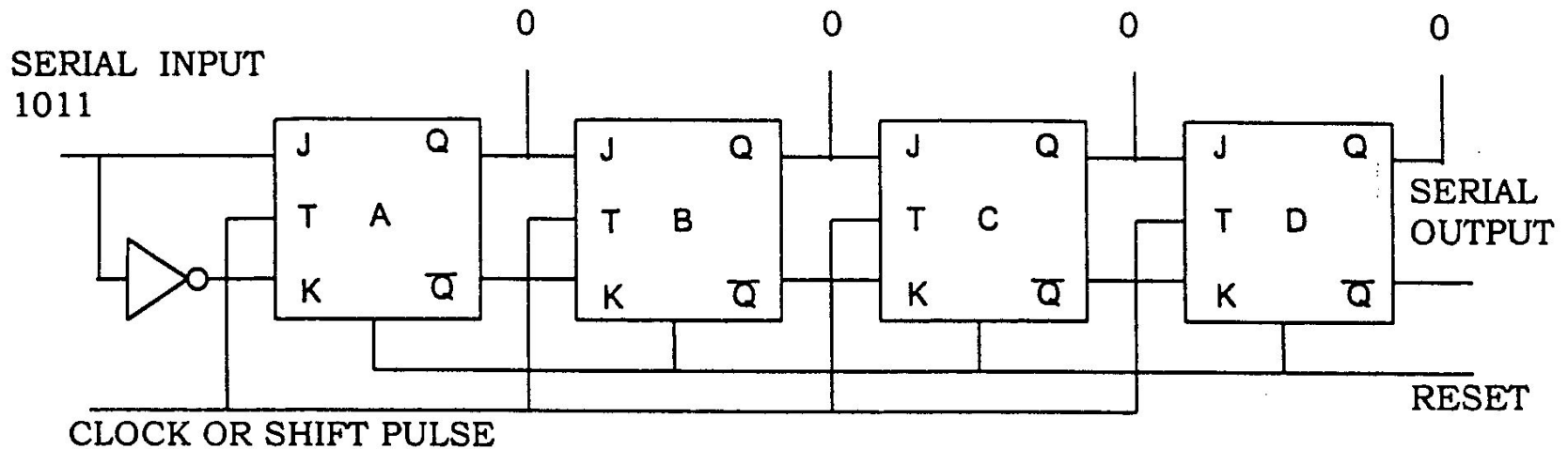


FOUR BIT SHIFT REGISTER

Используется для хранения данных.

После каждого импульса содержание регистра смещается на одно место вправо

ENCODER- ШИФРАТОР

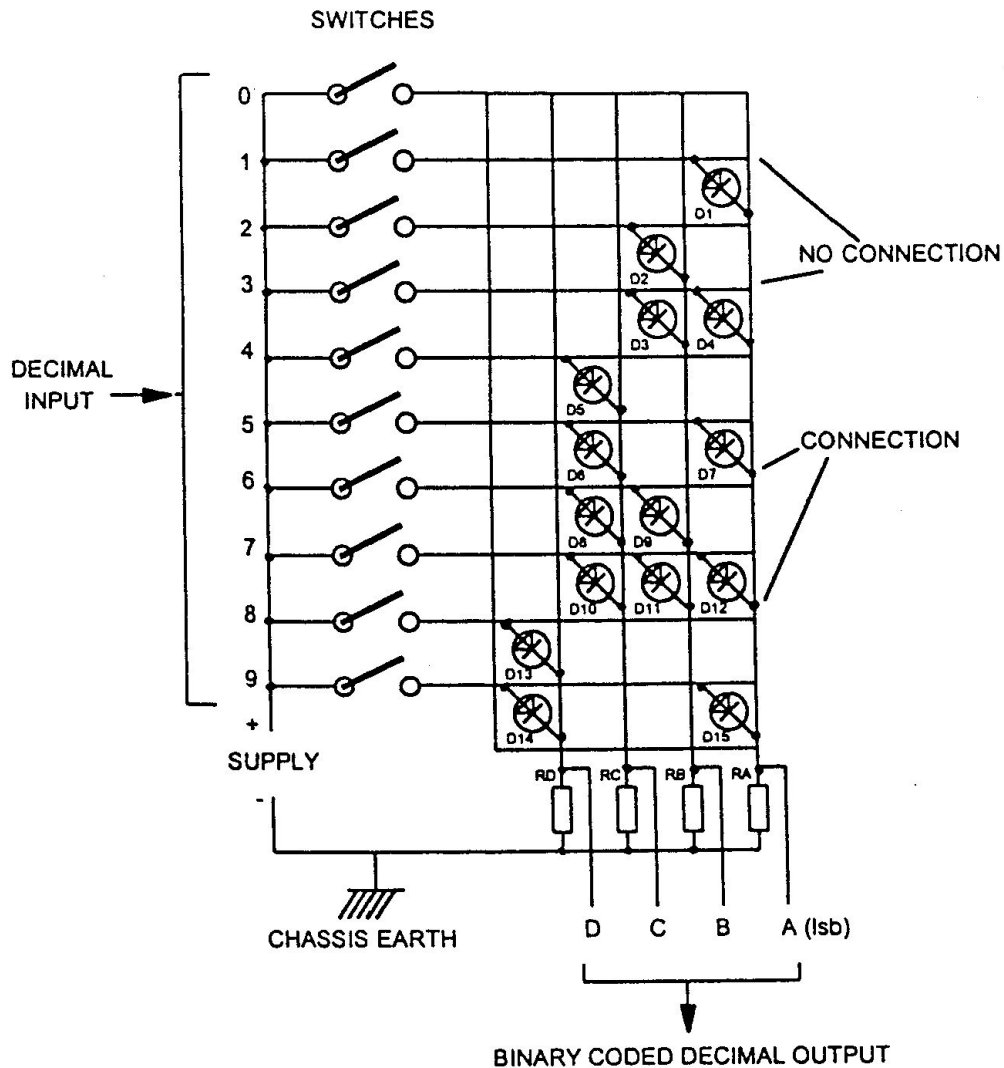



DECIMAL TO BCD ENCODER

Примеры использования

This principle will be employed in INS (Inertial Navigation Systems), IRS (Inertial Reference Systems) and FMS (Flight Management Systems) as all these have keyboards. So some form of encoding will convert the input signals into the correct code for the system.

INS , IRS , FMS и др

 

 

LINE
SELECT
KEYS

SCRATCH
PAD

DISPLAY
LIGHT


FAIL
LIGHT

TITLE

MESSAGE
LIGHT


OFFSET
LIGHT

CDU FMS

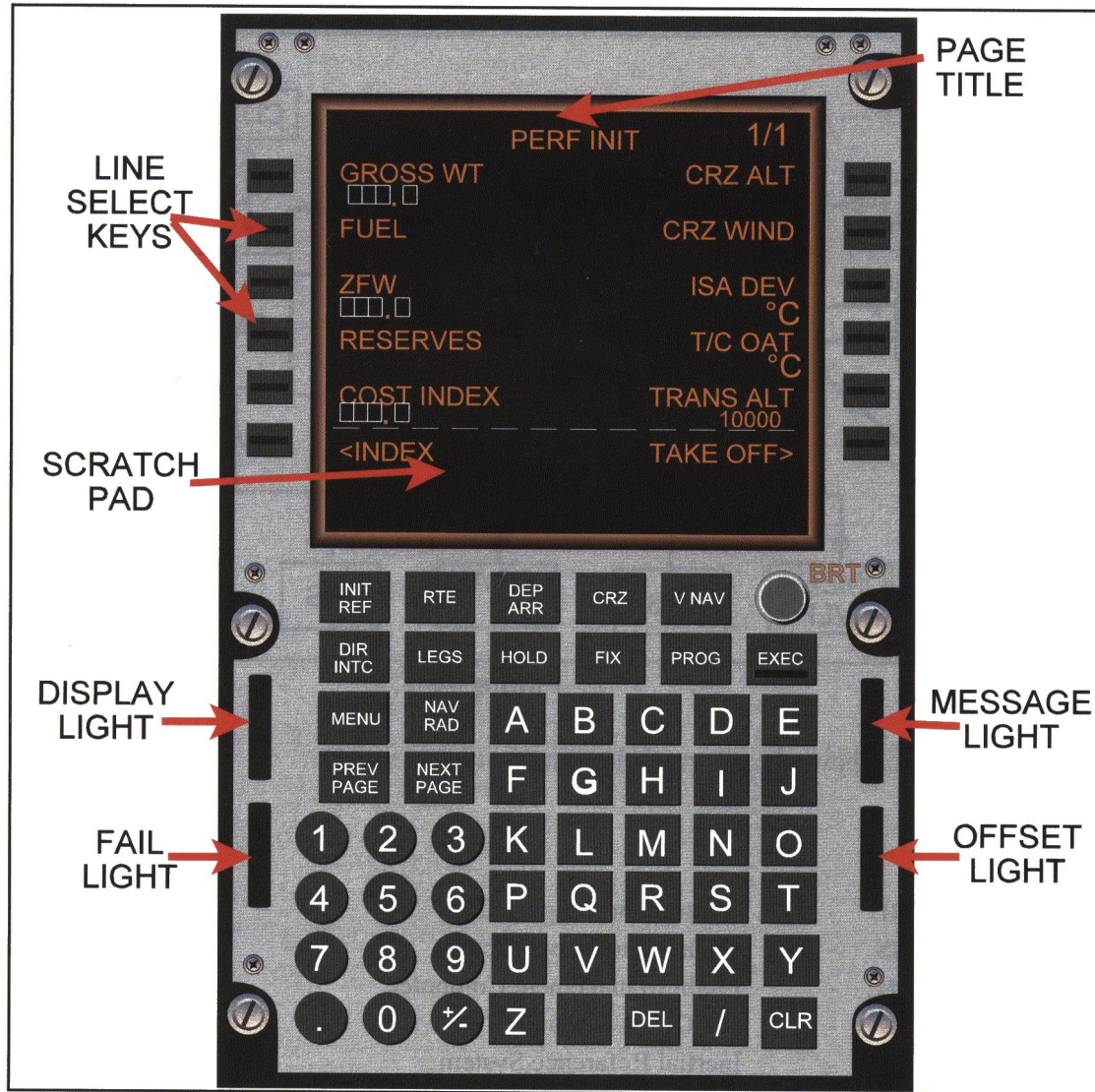

Аналого-цифровое преобразование без обратной связи


Компаратор

 

Входное напряжение	Логический выход
$U_A > U_B$	$Q=1$
$U_A < U_B$	$Q=0$
$U_A = U_B$	Предыдущее состояние

Аналого-цифровое преобразование без обратной связи

Компаратор

 


Входное напряжение	Логический выход
$U_A > U_B$	$Q=1$
$U_A < U_B$	$Q=0$
$U_A = U_B$	Предыдущее состояние

АЦП считывания (Flash Convertor)

Таблица выходов

Входное напряжение	Выходы компараторов									Выходы шифратора			Over-flow
	Q ₈	Q ₇	Q ₆	Q ₅	Q ₄	Q ₃	Q ₂	Q ₁	Q ₀	B ₂	B ₁	B ₀	
меньше 0 В	0	0	0	0	0	0	0	0	0	0	0	0	0
0 < U < 1,25 В	0	0	0	0	0	0	0	0	1	0	0	0	0
1,25 < U < 2,5 В	0	0	0	0	0	0	0	1	1	0	0	1	0
2,5 < U < 3,75 В	0	0	0	0	0	0	1	1	1	0	1	0	0
3,75 < U < 5,0 В	0	0	0	0	0	1	1	1	1	0	1	1	0
5,0 < U < 6,25 В	0	0	0	0	1	1	1	1	1	1	0	0	0
6,25 < U < 7,5 В	0	0	0	1	1	1	1	1	1	1	0	1	0
7,5 < U < 8,75 В	0	0	1	1	1	1	1	1	1	1	1	0	0
8,75 < U < 10,0 В	0	1	1	1	1	1	1	1	1	1	1	1	0
10,0 < U	1	1	1	1	1	1	1	1	1	0	0	0	1

АЦП (ADC)

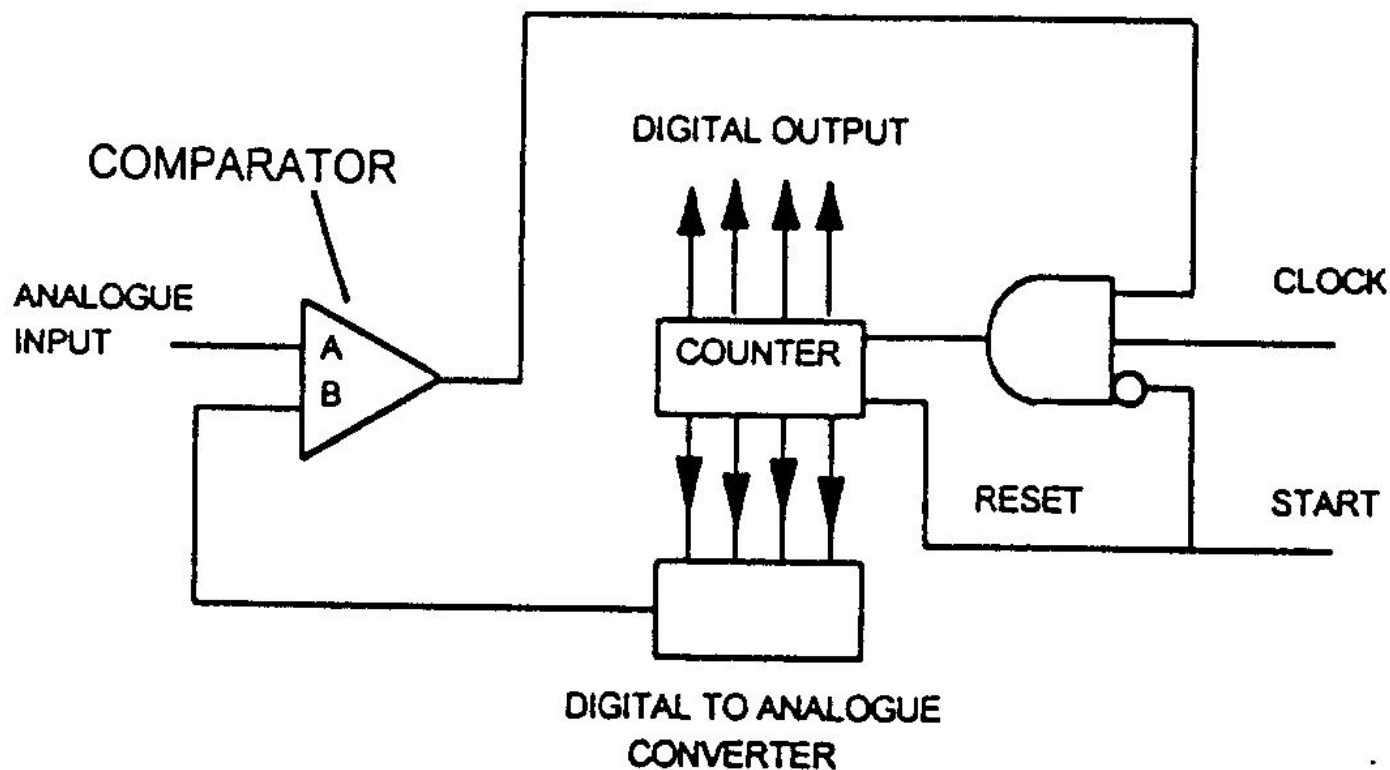

ANALOGUE TO DIGITAL CONVERTER

АЦП (ADC)

A comparator is a device with two inputs which compare the voltages at each input to determine which is greater, the output is logic 1 if A is larger than B and logic 0 if input B is larger than A. On start B is 0, A is the larger output, from the comparator is logic state 1 and when the START pulse goes low the AND gate 'opens' and the clock pulses go to the counter. Each pulse causes the counter to advance.

As the counter counts up, its value is converted into its analogue equivalent by the digital to analogue convertor (DAC or D to A or D/A) and applied to the comparator at B. The DAC output therefore increases in steps until it reaches just above the analogue input level ie, B input > A. The comparator output goes low, AND gate closes, the count stops, the digital read-out is then taken from the counter.


АЦП (ADC)

The best approximation we can obtain, depends on how much input B has to be greater than A ie, the step size, this is known as the quantization error. This type of Analogue to Digital (ADC or A to D or A/D) converter is slow in operation and is unsuitable for high speed operation, and of course the larger the voltage the longer (more steps) time it takes. The comparator would be an operational amplifier (see JAR Module 4).

This problem can be partly overcome by using an up/down counter. It counts up when the comparator is logic 1 and down when the comparator output is logic 0. As the analogue input varies it simply counts up or down from the previous count rather than re-setting to zero as did the digital ramp convertor. This type is called the continuous digital-ramp convertor and is a considerable improvement on the previous one.

However, the fastest type of ADC of the ones considered is the successive approximation type.

АЦП-

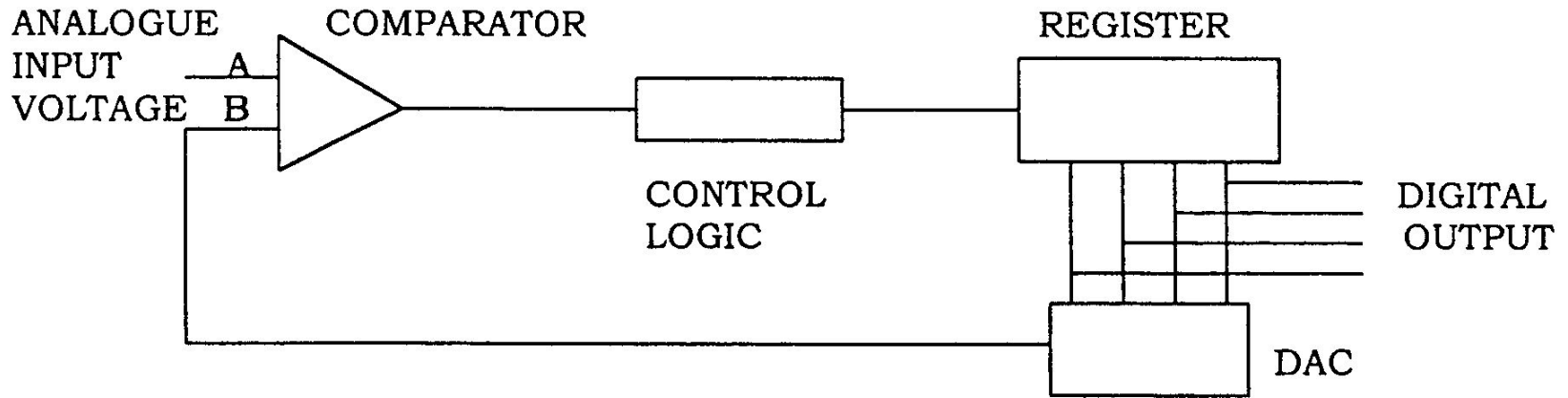

SUCCESSIVE APPROXIMATION TYPE OF D TO A CONVERTER

AЦП-

SUCCESSIVE APPROXIMATION TYPE OF D TO A CONVERTER


This is similar to the previous circuit but the register is used instead of a counter and a control logic block is included between the comparator and register, which controls the output of the register.

Initially a reset signal puts all bits in the register to 0. The control logic sets the MSB in the register to 1 and the rest to logic 0. The output of the DAC is then compared to the analogue input if $B > A$ then this number is too large and the MSB remains at 1.

At the next clock pulse the control changes the next bit in the register $B > A$ it is set to 0 if $B < A$ it is set to 1 and so on until all the bit values are found. The digital read out can then be read.


This has a fast conversion time which does not depend on the analogue voltage level but just the number of bits in the convertor.

DECODER- ДЕШИФРАТОР

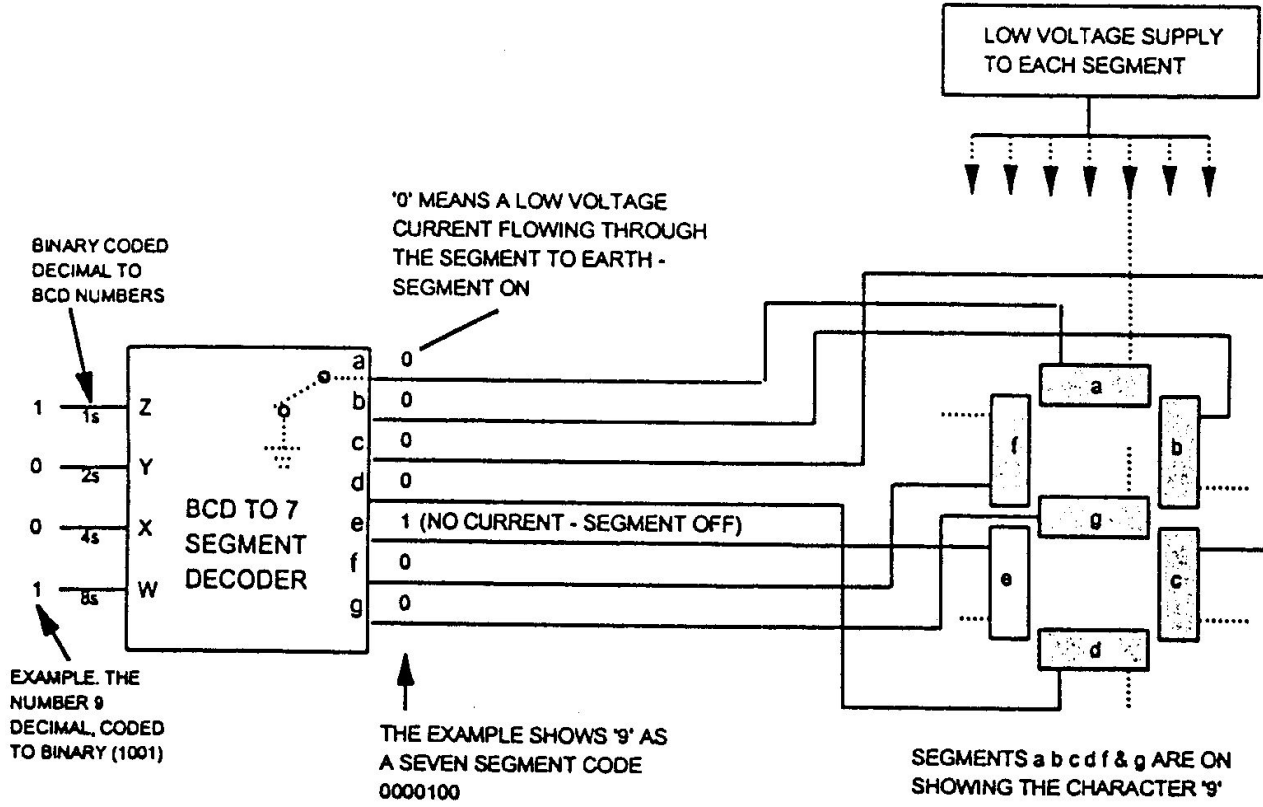


BCD TO SEVEN SEGMENT DECODER

Примеры использования

 

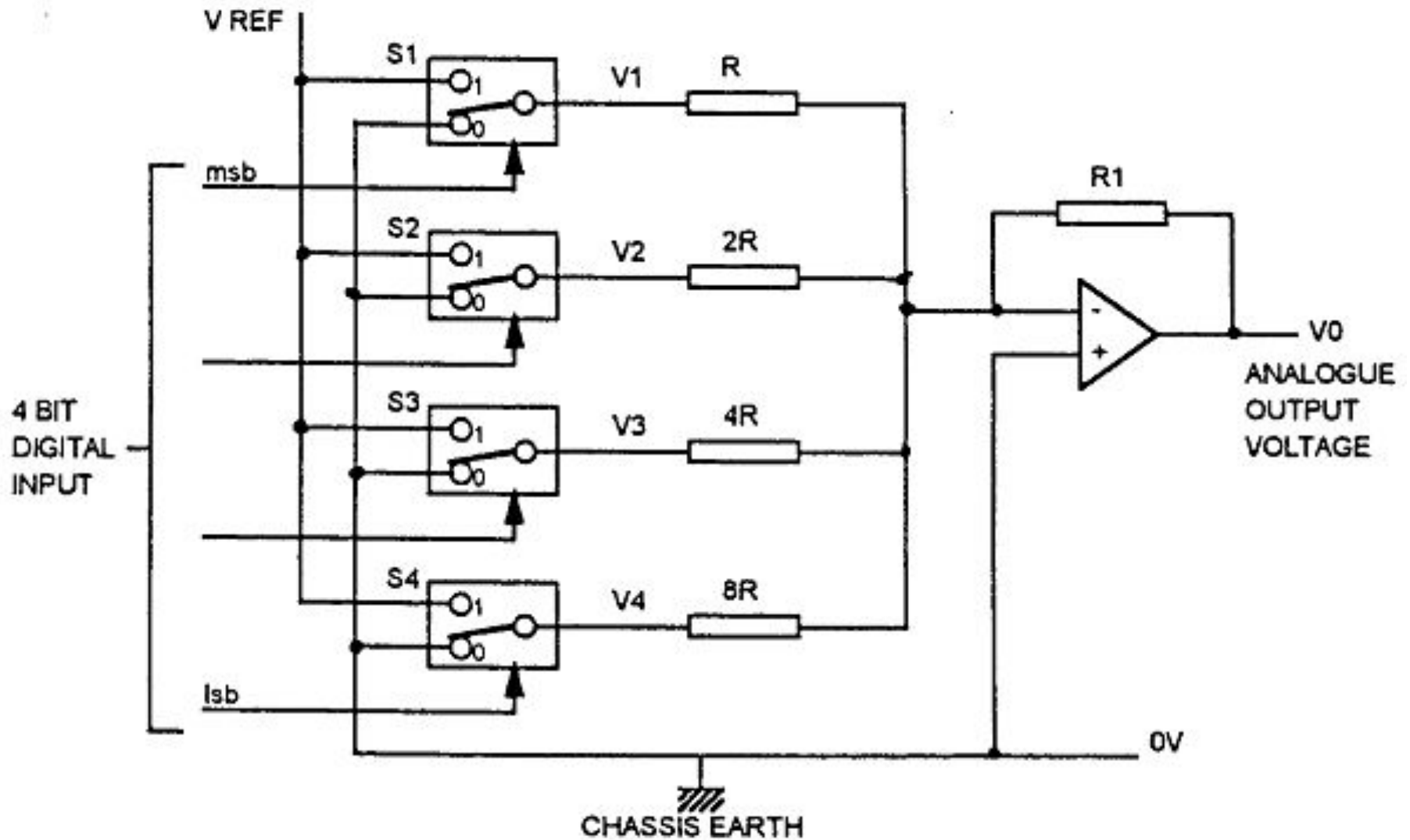ЦАП (DAC) – Цифро-аналоговый преобразователь



ЦАП (DAC) – Цифро-аналоговый преобразователь

Digital to Analogue Converter

The next drawing shows a binary weighted resistor method, so called as the values of the resistors increase in accordance with the binary system eg, R, 2R, 4R, 8R. The output from the resistor chain is connected to an operational amplifier as a summing amplifier with a feedback resistor R_f . The output V_0 is therefore $V_0 = -R_f \left(\frac{V_1}{R} + \frac{V_2}{2R} + \frac{V_3}{4R} + \frac{V_4}{8R} \right)$ (see JAR Module 4)

Also in the circuit are four switches S, S_1 , S_2 , S_3 , S_4 which are electronic switches (digitally controlled). Each switch connects the resistor to a fixed reference V_{ref} when the input bit is logic 1 (+5v) and to ground (0v) when the input bit is logic 0.

Assuming that $R_f = R = 1K$ then the output formula becomes:

$$V_0 = - \left(\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{8} \right)$$

If the input number is 0001 then:

$$V_1 = V_2 = V_3 = 0$$

ЦАП (DAC) – Цифро-аналоговый преобразователь

ie each of the electronic switches connecting the input to ground.

V_4 will be connected to V_{ref} , we will assume that V_{ref} is $-8v$ so the formula becomes:

$$V_0 = - \left(0 + 0 + 0 + \frac{-8}{8} \right)$$

$$V_0 = + 1v$$

Note. With the example shown the output was positive but if V_{ref} was $+8v$ then the output would be $-1v$.

With an input of 0100 $V_1 = V_3 = V_4 = 0$


$V_2 = V_{ref}$. Assume again $V_{ref} = -8v$

$$V_0 = - \left(\frac{-8}{2} \right) = + 4v$$

$$V_0 = \left(0 + \frac{-8}{2} + 0 + 0 \right)$$

As you can see the weighting of the LSB is $1v$ in this case.

R-2R Type D to A Converter

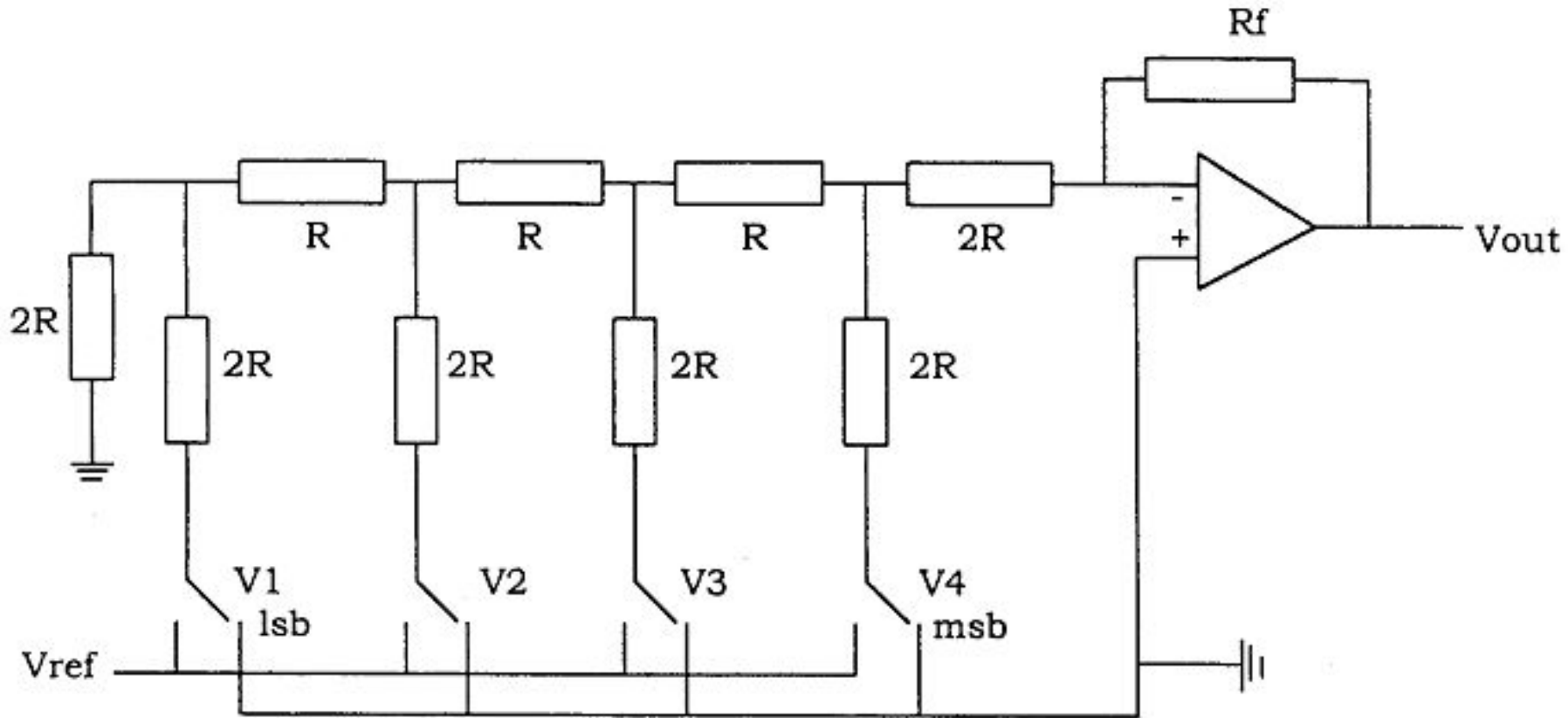

Another problem is the larger the bit word the more the range of resistors is required ie, for every extra bit the range of the required resistors doubles. So another method of converting digital to analogue must be found for digital words with a large number of bits - it is called the R - 2R type.

R-2R Type D to A Convertor

The circuit works on the principle that a pair of 2R resistors at the end of the ladder can be considered in parallel, forming an overall resistance R.

This system does use twice the number of resistors compared to the binary weighted network, but the use of only two values of resistors means the system can handle any number of input bits, simply by extending the resistor ladder.

It is not essential you know the full operation of this DAC but you should know it exists.

With reference to the drawing above $V_{out} = \frac{V}{16} \cdot \frac{R_f}{R} (8v_4 + 4v_3 + 4v_2 + 4v_1)$ for the bit input shown.